

EECE 2322 Fall 2023 Homework 1

Jason Martinez

September 20, 2023

Questions

- (a) (2 pts) Derive the outputs $F1$ and $F2$ as Boolean functions of the four inputs A , B , C , and D , as implemented in the circuit.

(a) $F_1 = [A \vee [\neg B \wedge C]] \vee [D \oplus [\neg A \wedge B]]$

(b) $F_2 = \neg A \wedge B$

- (b) (2 pts) List the truth table for the four input variables. Then determine and list the binary values for $T1$ through $T4$ and outputs $F1$ and $F2$ in the table.

A	B	C	D	T_1	T_2	T_3	T_4	F_1	F_2
1	1	1	1	0	0	1	1	1	0
1	1	1	0	0	0	1	0	1	0
1	1	0	1	0	0	1	1	1	0
1	1	0	0	0	0	1	0	1	0
1	0	1	1	1	0	1	1	1	0
1	0	1	0	1	0	1	0	1	0
1	0	0	1	0	0	1	1	1	0
1	0	0	0	0	0	1	0	1	0
0	1	1	1	0	1	0	1	0	1
0	1	1	0	0	1	0	0	1	1
0	1	0	1	0	1	0	1	0	1
0	1	0	0	0	1	0	0	1	1
0	0	1	1	1	0	1	1	1	0
0	0	1	0	1	0	1	0	1	0
0	0	0	1	0	0	0	1	1	0
0	0	0	0	0	0	0	0	0	0

- (c) (3 pts) Complete two separate 4-input K-Maps, one for each of the outputs $F1$ and $F2$. Simplify with the K-Maps and show the final Boolean expressions for the two outputs.
- (d) (2 pts) Redesign the simplified output $F1$ with all NAND gates.
- (e) (2 pts) Redesign the simplified output $F2$ with all NOR gates.
- (f) (2 pts) Write a SystemVerilog module for the output $F1$ only as implemented in the circuit design given above using the Boolean expression from part (a) above with Behavioral continuous model.
- (g) (2 pts) Write a SystemVerilog module (using structural model) of the output $F1$ circuit implemented with all NAND gates in part (d) above in the same SystemVerilog design file used in part (f).
- (h) (2 pts) Write an appropriate test-bench for the two module circuits above that tests the correct behavior and similarity of your design for the given combination of the inputs.
- (i) (3 pts) Simulate your SystemVerilog design with Xilinx Vivado and show the screen capture of both the terminal output (\$monitor task) and waveform output of the simulation verifying correct behavior from both modules.